

CSE-308: Digital System Design

Lecture 2

Description Styles in Verilog

- Two different styles of description:
 1. Data flow
 - Continuous assignment
 2. Behavioral
 - Procedural assignment
 - ❖ Blocking //
 - ❖ Non-blocking //

assign



Data-flow Style: Continuous Assignment

- Identified by the keyword "assign".

assign a = b & c;

assign f[2] = c[0];



- Forms a static binding between
 - The 'net' being assigned on the LHS,
 - The expression on the RHS.
- The assignment is continuously active.
- Almost exclusively used to model combinational logic.

- A Verilog module can contain any number of continuous assignment statements.
- For an “assign” statement,
 - The expression on RHS may contain both “register” or “net” type variables.
 - The LHS must be of “net” type, typically a “wire”.
- Several examples of “assign” illustrated already.


assign b = <exp>;

```

module generate_mux (data, select, out);
  input [0:7] data;
  input [0:2] select;
  output out;

  assign out = data [ select];
endmodule

```

 

$out = data[2];$


Non-constant index in
expression on RHS
generates a MUX


```

module generate_decoder (out, in, select);
  input in;
  input [0:1] select;
  output [0:3] out;

  assign out [ select ] = in;
endmodule

```

 


Non-constant index in
expression on LHS
generates a decoder

```

module level_sensitive_latch (D, Q, En);
  input D, En;
  output Q;


  assign Q = en ? D : Q;
endmodule

```

 

Using “assign” to describe sequential logic

 assign $a = b$
assign $b = c$
assign $c = a$



Behavioral Style: Procedural Assignment

- The procedural block defines
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.
- Two types of procedural blocks in Verilog
 - The "always" block ✓
 - A continuous loop that never terminates.
 - The "initial" block ✓
 - Executed once at the beginning of simulation (used in Test-benches).

© CEF
L.L.T. KGP[illegible]

Behavioral Style: Procedural Assignment

- The procedural block defines
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.
- Two types of procedural blocks in Verilog
 - The "always" block ✓
 - A continuous loop that never terminates.
 - The "initial" block ✓
 - Executed once at the beginning of simulation (used in Test-benches).

- A module can contain any number of “always” blocks, all of which execute concurrently.
- Basic syntax of “always” block:

```
always @(event_expression)
begin
    statement;
    statement;
end
```

} Sequential statements

- The @(event_expression) is required for both combinational and sequential logic descriptions.

- Only “reg” type variables can be assigned within an “always” block.
Why??

- The sequential “always” block executes only when the event expression triggers.
- At other times the block is doing nothing.
- An object being assigned to must therefore remember the last value assigned (not continuously driven).
- So, only “reg” type variables can be assigned within the “always” block.
- Of course, any kind of variable may appear in the event expression (reg, wire, etc.).

Sequential Statements in Verilog

© GET KGP

1. begin

 sequential_statements

end

2. if (expression)

 sequential_statement

 [else

 sequential_statement]

3. case (expression)

 expr: sequential_statement

 default: sequential_statement

endcase

begin...end
not required
if there
is only 1 stmt.

4. forever
 sequential_statement }
5. repeat (expression)
 sequential_statement }
6. while (expression)
 sequential_statement }
7. for (expr1; expr2; expr3)
 sequential_statement }

repeat(10)
{

}

8. # (time_value)

- Makes a block suspend for "time_value" time units.

9. @ (event_expression)

- Makes a block suspend until event_expression triggers.

20



// A combinational logic example

© GET
I.I.T. KGP

```
module mux21 (in1, in0, s, f);
```

```
  input in1, in0, s;
```

```
  output f;
```

```
  reg f;
```

```
  always @ (in1 or in0 or s)
```



```
    if (s)
```

```
      f = in1;
```

```
    else
```

```
      f = in0;
```

```
endmodule
```

  


// A sequential logic example

© GATE
L.T. KGP

```
module dff_negedge (D, clock, Q, Qbar);  
  input D, clock;  
  output Q, Qbar;  
  reg Q, Qbar;
```
 
```
  always @ (negedge clock)  
  begin  
    Q = D;  
    Qbar = ~D;  
  end  
endmodule
```



// Another sequential logic example

© G.L.T.
L.T.T. KGP

```
module incomp_state_spec (curr_state, flag);
```

```
  input  [0:1] curr_state;
```

```
  output [0:1] flag;
```

```
  reg    [0:1] flag;
```

```
  always @ (curr_state)
```


```
    case (curr_state)
```

```
      0, 1 : flag = 2;
```

```
      3    : flag = 0;
```

```
    endcase
```

```
endmodule
```

 

The variable 'flag' is not
assigned a value in all the
branches of case.

→ Latch is *inferred*

// A small change made

© GATE
I.I.T. KGP

```
module incomp_state_spec (curr_state, flag);  
  input  [0:1] curr_state;  
  output [0:1] flag;  
  reg     [0:1] flag;
```

```
  always @ (curr_state)  
begin  flag = 0;
```

```
    case (curr_state)
```

```
      0, 1 : flag = 2; break
```

```
      3    : flag = 0; break
```


```
end  _endcase  
endmodule
```



'flag' defined for all
values of curr_state.

→ Latch is avoided
 
```
module ALU_4bit (f, a, b, op);  
    input [1:0] op;    input [3:0] a, b;  
    output [3:0] f;    reg [3:0] f;  
    parameter ADD=2'b00, SUB=2'b01,  
              MUL=2'b10, DIV=2'b11;  
    always @(a or b or op)  
        case (op)  
            ADD : f = a + b;  
            SUB : f = a - b;  
            MUL : f = a * b;  
            DIV : f = a / b;  
        endcase  
endmodule
```



module priority_encoder (in, code);

input [0:3] in;

output [0:1] code;

reg [0:1] code;

always @(in)

case (1'b1)

input[0] : code = 2'b00;


input[1] : code = 2'b01;

input[2] : code = 2'd10;

input[3] : code = 2'b11;

endcase

endmodule

 

0
0
0
0