

No:

Date:

Pdt: 3-10-2021

Name: Shah Raza

Reg No: 18PWCSE1658

Section: B

Subject: DSD

Assignment No: 1

No:


Date:

PROBLEM 1: Draw the logic circuit described by the verilog code below.

```
module pie(x,y,a,b,c);  
  input a,b,c;  
  output x,y;  
  wire t1,t2;  
  xor x1(t1,a,b);  
  not n1(x,t1);  
  and a1(t2,x,c);  
  or o1(y,t2,b);  
endmodule
```

~~Qata~~

SOLUTION:

 

No:

Date:

PROBLEM 3:

PART:

```
module part(x, y, a, b, c);  
    input a, b, c;  
    output x, y;  
    wire bnot;
```

```
    and a1(x, a, bnot);  
    or o1(y, x, c);
```

```
endmodule
```

WHOLE:

```
module whole(x, y, a, b, c);  
    input [2:0] a, b;  
    output [2:0] x;  
    input c;  
    output y;  
    wire w1, w2;
```

```
    part p1(x[0], w1, a[0], b[0], c);
```

```
    part p2(x[1], w2, a[1], b[1], w1);
```

```
    part p3(x[2], y, a[2], b[2], w2);
```


```
endmodule
```




No:

Date:


## PROBLEM 2:

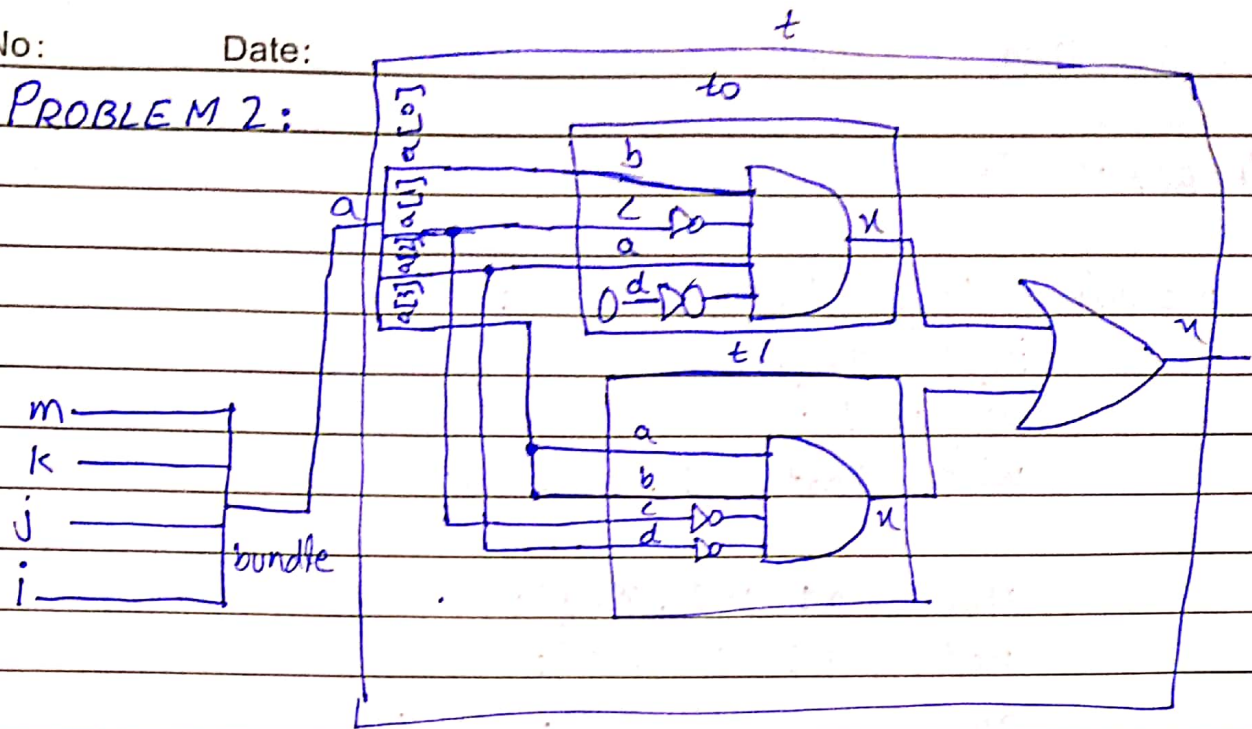


## PROBLEM 4:

 a) assign  $x = a \% b ? 1 : 0;$ 

and a1(x, a, b);

 b) assign  $x = a == b ? 0 : 1;$ 

xor x1(x, a, b);

 c) assign  $x = a ? b : c;$ 

wire anot, w1, w2;

and a1(w1, a, b);

not n1(anot, a);

and a2(w2, anot, c);

or o1(x, w1, w2);

No:

Date:

### PROBLEM 5:

```
module Logic(F, x, y, Z, w);  
    input x, y, Z, w;  
    output F;  
    wire Znot, w1, w2, w3;  
  
    and a1(w1, x, y);  
    not n1(Znot, Z);  
    and a2(w2, x, y, Znot);  
    and a3(w3, x, y, w);  
    or o1(F, w1, w2, w3);  
endmodule
```

~~Qazew~~

### PROBLEM 6:

```
module Logic(F, x, y, Z, w);  
    input x, y, Z, w;  
    output F;  
    assign F = (x & y) | (x & y & (~Z)) | (x & y & w);  
endmodule
```