

*Name: Solution

*Registration: _____

Department of Computer Systems Engineering
University of Engineering & Technology Peshawar

Digital System Design

CSE 308

Midterm Examination Spring 2016

1 April 2016, Duration: 120 Minutes

Exam Rules

Please read carefully before proceeding.

- 1- This exam is open books/notes but closed laptops/Internet.
- 2- No calculators/mobiles of any kind are allowed.
- 3- It's good to share but sharing of books, notes, and other materials during this exam is not permitted.
- 4- There are 4 problems in total. Some problems are harder than others. Answer the easy ones first to maximize your score.
- 5- This exam booklet contains 13 pages, including this cover.
Count them to be sure you have them all.

Problem 1 _____ (15 pts)

Problem 2 _____ (15 pts)

Problem 3 _____ (50 pts)

Problem 4 _____ (20 pts)

Exam Total _____ (100 pts)

Good Luck!

Problem 1: (15 pts)

(a) (5 pts)

1. y has to be defined as reg
2. y and z must not be in the trigger list
3. s must be in the sensitivity list


(b) (5 pts)

Yes. 2 latches

One to store previous value of z , when $s = 0$ ($y = x$).


One to store previous value of y , when $s = 1$ ($z = x$).

(c) (5 pts)

 

Problem 2: (15 pts)

(a) (8 pts)

 

(b) (7 pts)

```
`timescale 1ns / 1ns
module clk_gen;
    reg clk;

    initial
    begin
        clk = 1'b0;
        forever
            begin
                #15 clk = ~ clk;
                #5  clk = ~ clk;
            end
    end
end
endmodule
```

Problem 3: (50 pts)

(a) Module 1: Gray Counter. (10 pts)

```
module GRAY_CNT (
    CLK,
    RESET,
    GRAY_OUT);

    input CLK;
    input RESET;
    output [2:0] GRAY_OUT;

    reg [2:0] GRAY_OUT;

    always @ (posedge CLK)
        if (RESET)
            GRAY_OUT = 3'b000;
        else
            case (GRAY_OUT)
                3'h0: GRAY_OUT = 3'h1;
                3'h1: GRAY_OUT = 3'h3;
                3'h3: GRAY_OUT = 3'h2;
                3'h2: GRAY_OUT = 3'h6;
                3'h6: GRAY_OUT = 3'h7;
                3'h7: GRAY_OUT = 3'h5;
                3'h5: GRAY_OUT = 3'h4;
                3'h4: GRAY_OUT = 3'h0;
                default: GRAY_OUT = 3'h0;
            endcase
endmodule
```

(b) Module 2: Parallel-in, Serial-out Shift Register. (10 pts)

```
module PISO_SHIFT (
    CLK,
    LD,
    SHIFT,
    PI,
    Q);

    input CLK;
    input LD;
    input SHIFT;
    input [7:0] PI;
    output Q;

    reg Q;
    reg [7:0] SHIFTER;

    always @ (posedge CLK)
        if (LD)
            SHIFTER = PI;
        else if (SHIFT)
            begin
                Q = SHIFTER[7];
                SHIFTER = {SHIFTER[6:0], 1'b0};
            end
    end

endmodule
```

(c) Module 3: Up-Down, Loadable Counter. (10 pts)

```
module UP_DN_LD_CNT (
    CLK,
    RESET,
    UP_DN,
    LD,
    DIN,
    Q);
    input CLK;
    input RESET;
    input UP_DN;
    input LD;
    input [2:0] DIN;
    output [2:0] Q;

    reg [2:0] Q;

    always @ (negedge CLK)
        if (~RESET)
            Q = 3'b011;
        else
            if (LD)
                Q = DIN;
            else if (UP_DN)
                Q = Q + 1;
            else
                Q = Q - 1;
endmodule
```

(d) Module 4: Multiplexer. (10 pts)


```
module MUX_8 (  
    SEL,  
    D0,  
    D1,  
    D2,  
    D3,  
    D4,  
    D5,  
    D6,  
    D7,  
    O);  
  
    input [2:0] SEL;  
    input [7:0] D0;  
    input [7:0] D1;  
    input [7:0] D2;  
    input [7:0] D3;  
    input [7:0] D4;  
    input [7:0] D5;  
    input [7:0] D6;  
    input [7:0] D7;  
    output [7:0] O;  
  
    reg O;  
  
    always @ (*)  
        case (SEL)  
            3'b000: O = D0;  
            3'b001: O = D1;  
            3'b010: O = D2;  
            3'b011: O = D3;  
            3'b100: O = D4;  
            3'b101: O = D5;  
            3'b110: O = D6;  
            3'b111: O = D7;  
        endcase  
endmodule
```

(e) Top-Level Design. (10 pts)

```
module TOP (  
    CLK,  
    RESET,  
    OUT_DATA,  
    IN0,  
    IN1,  
    IN2,  
    IN3,  
    IN4,  
    IN5,  
    IN6,  
    IN7);  
  
    input CLK, RESET;  
    input [7:0] IN0;  
    input [7:0] IN1;  
    input [7:0] IN2;  
    input [7:0] IN3;  
    input [7:0] IN4;  
    input [7:0] IN5;  
    input [7:0] IN6;  
    input [7:0] IN7;  
    output [7:0] OUT_DATA;  
  
    wire [7:0] GRAYOUT;  
  
    GRAY_CNT GRAYCNT_INST1 (CLK, RESET, GRAYOUT);  
    MUX_8 MUX8_INST1 (GRAYOUT, IN0, IN1, IN2, IN3, IN4, IN5, IN6, IN7,  
    OUT_DATA);  
  
endmodule
```


Problem 4: (20 pts)

(a) (5 pts)

 

(b) (5 pts)

Moore/Mealy machine (1pt): Moore machine

Justification (4 pts): This is a Moore machine because the output (location) can be determined from the state.

(c) (10 pts)

```
module PEER (
    CLK,
    RESET,
    MOVE,
    STATE);

    input CLK, RESET, MOVE;
    output reg [2:0] STATE;

    always @ (posedge CLK)
        begin
            if (RESET)
                STATE <= 3'b000;
            else
                case (STATE)
                    3'b000: STATE <= MOVE ? 3'b001 : 3'b000;
                    3'b001: STATE <= MOVE ? 3'b100 : 3'b010;
                    3'b010: STATE <= MOVE ? 3'b100 : 3'b011;
                    3'b011: STATE <= MOVE ? 3'b000 : 3'b011;
                    3'b100: STATE <= MOVE ? 3'b101 : 3'b111;
                    3'b101: STATE <= MOVE ? 3'b110 : 3'b011;
                    3'b110: STATE <= MOVE ? 3'b110 : 3'b111;
                    3'b111: STATE <= MOVE ? 3'b101 : 3'b001;
                    default: STATE <= 3'b000;
                endcase
            end
        end
endmodule
```