

CSE-308: Digital System Design

# Lecture 5

## Blocking & Non-blocking Assignments

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
  - Blocking assignment
    - Uses the ‘=’ operator
  - Non-blocking assignment
    - Uses the ‘<=’ operator

## Blocking Assignment (using ' $=$ ')<sup>GLT KCP</sup>

- Most commonly used type.
- The target of assignment gets updated before the next sequential statement in the procedural block is executed.
- A statement using blocking assignment blocks the execution of the statements following it, until it gets completed.
- Recommended style for modeling combinational logic.

$f = a + b;$

## Non-Blocking Assignment (using ' $\leq$ ')

- The assignment to the target gets scheduled for the end of the simulation cycle.
  - Normally occurs at the end of the sequential block.
  - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
  - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.



simulatorsim.  
cycle

always @ (posedge. -)

begin

f &lt;=

—f

g &lt;=

-f—

h &lt;=

—

end

## Non-Blocking Assignment (using '<=')

- The assignment to the target gets scheduled for the end of the simulation cycle.
  - Normally occurs at the end of the sequential block.
  - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
  - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.

## Some Rules to be Followed

- Verilog synthesizer ignores the delays specified in a procedural assignment statement.
  - May lead to functional mismatch between the design model and the synthesized netlist.
- A variable cannot appear as the target of *both* a blocking and a non-blocking assignment.
  - Following is not permissible:

```
value = value + 1;  
value<= init;
```


#10
 
#20



// Up-down counter (synchronous clear)


```
module counter (mode, clr, ld, d_in, clk, count);  
  input mode, clr, ld, clk;   input [0:7] d_in;  
  output [0:7] count;         reg [0:7] count;  
  always @ (posedge clk)  
    if (ld)  
      count <= d_in;  
    else if (clr)  
      count <= 0;  
    else if (mode)  
      count <= count + 1;  
    else  
      count <= count + 1;  
endmodule
```






// Parameterized design:: an  $N$ -bit counter
 
```
module counter (clear, clock, count);  
    parameter N = 7;  
    input clear, clock;  
    output [0:N] count;      reg [0:N] count;  
  
    always @(negedge clock)  
    if (clear)  
        count <= 0;  
    else  
        count <= count + 1;  
endmodule
```



// Using more than one clocks in a module
 
```
module multiple_clk (clk1, clk2, a, b, c, f1, f2);  
  input clk1, clk2, a, b, c;  
  output f1, f2;  
  reg f1, f2;  
  always @(posedge clk1)   
    f1 <= a & b;  
  always @(negedge clk2)   
    f2 <= b ^ c;  
endmodule
```



// Using multiple edges of the same clock

```
module multi_phase_clk (a, b, f, clk);
```

```
  input a, b, clk;
```

```
  output f;
```

```
  reg f, t;
```


```
  always @ (posedge clk)
```

```
    f <= t & b;
```

```
  always @ (negedge clk)
```

```
    t <= a | b;
```

```
endmodule
```


 



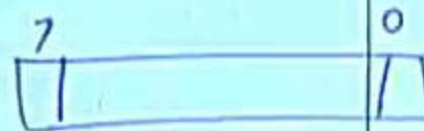 
## A Ring Counter Example

© CEC  
I.I.T. KGP

```
module ring_counter (clk, init, count);  
  input clk, init;    output [7:0] count;  
  reg [7:0] count;  
  always @ (posedge clk)  
  begin  
    if (init)  
      count = 8'b10000000;  
    else begin  
      count = count << 1;  
      count[0] = count[7];  
    end  
  end  
endmodule
```



## A Ring Counter Example (Modified--1)

© CET  
U.T. KGP

```
module ring_counter_modi1 (clk, init, count);  
  input clk, init;    output [7:0] count;  
  reg [7:0] count;  
  always @ (posedge clk)  
  begin  
    if (init)  
      count = 8'b10000000;  
    else begin  
      count <= count << 1;  
      count[0] <= count[7];  
    end  
  end  
end  
endmodule
```


10000000

count <= count << 1;  
count[0] <= count[7];
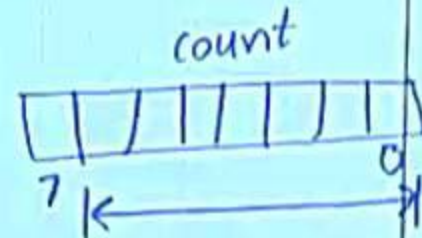
## A Ring Counter Example (Modified - 2)

© GET  
L.T. KGP

```
module ring_counter_modi2 (clk, init, count);  
  input clk, init;    output [7:0] count;  
  reg [7:0] count;  
  always @ (posedge clk)  
  begin  
    if (init)  
      count = 8'b10000000;  
    else  
      count = {count[6:0], count[7]};  
  endmodule
```



<<



## About “Loop” Statements


© CET  
J.J.T. KGP

- Verilog supports four types of loops:
  - ‘while’ loop ✓
  - ‘for’ loop ✓
  - ‘forever’ loop ✓
  - ‘repeat’ loop ✓
- Many Verilog synthesizers supports only ‘for’ loop for synthesis:
  - Loop bound must evaluate to a constant.
  - Implemented by unrolling the ‘for’ loop, and replicating the statements.
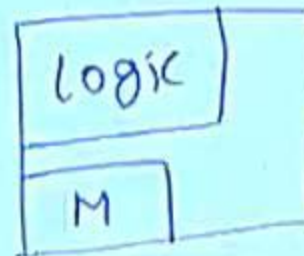
# Modeling Memory

© CBT  
LIT, RGP

- Synthesis tools are usually not very efficient in synthesizing memory.
  - Best modeled as a component.
  - Instantiated in a design.
- Implementing memory as a two-dimensional register file is inefficient.



```
module memory_example (en, clk, adbus, dbus,  
                        rw);  
  
    parameter N = 16;  
    input  en, rw, clk;  
    input [N-1:0] adbus;  
    output [N-1:0] dbus;  
  
    .....  
    ROM Mem1 (clk, en, rw, adbus, dbus);  
    .....  
endmodule
```



## Modeling Tri-state Gates

©CET  
I.I.T. KGP

```
module bus_driver (in, out, enable);  
  input enable;      input [0:7] in;  
  output [0:7] out;  reg [0:7] out;
```

```
  always @(enable or in)
```


```
    if (enable)
```

```
      out = in;
```

```
    else
```

```
      out = 8'bz;
```

```
endmodule;
```

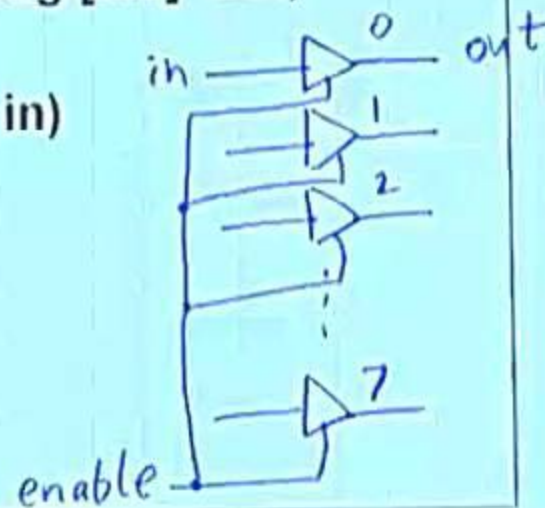


# Modeling Finite State Machines


© CEF  
I.I.T. KGP

- Two types of FSMs

- Moore Machine

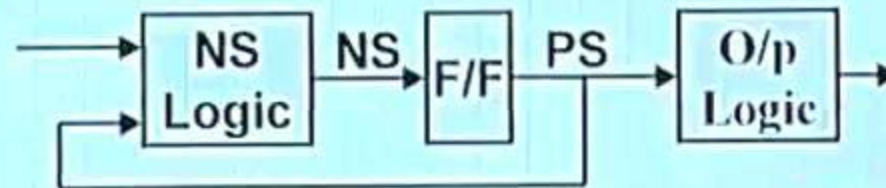

- Mealy Machine

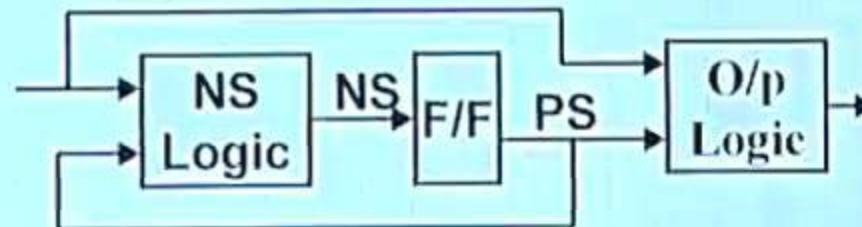

## Output logic :

- \* Latched
- \* Non-latched

