

No:

Date:


NAME : SHAH RAZA

REG No: 18PWCSE1658

SECTION: B

SUBJECT: DSD

ASSIGNMENT No: 3

Signature: 

No:


Date:

### PROBLEM 1:

Draw the synthesized circuits described by the verilog codes.

a)

Solution:

 


No:

Date:

b)

Solution:


~~Q20~~

 

smpl circuit

c)

Solution:

 

D-latch



**PROBLEM 2:**

Implement an 8-bit ripple carry adder, using as building block the 1-bit full adder from 1(a). Use the following module template for your top level design:

Solution:

~~Prize~~

```

module adder8(A, B, cin, S, cout);
    input [7:0] A, B;
    input cin;
    output [7:0] S;
    output cout;
    wire c1, c2, c3, c4, c5, c6, c7;

    FA fa0(A[0], B[0], cin, c1, S[0]);
    FA fa1(A[1], B[1], c1, c2, S[1]);
    FA fa2(A[2], B[2], c2, c3, S[2]);
    FA fa3(A[3], B[3], c3, c4, S[3]);
    FA fa4(A[4], B[4], c4, c5, S[4]);
    FA fa5(A[5], B[5], c5, c6, S[5]);
    FA fa6(A[6], B[6], c6, c7, S[6]);
    FA fa7(A[7], B[7], c7, cout, S[7]);
endmodule

```

No:

Date:

### PROBLEM 3:

Implement a 4-bit magnitude comparator using dataflow description (i.e using continuous assignment).

Solution:

```
module mag_comp4(A, B, ALB, AGB, AEB);  
    input [3:0] A, B;  
    output ALB, AGB, AEB;  
  
    assign ALB = (A < B);  
    assign AGB = (A > B);  
    assign AEB = (A == B);  
endmodule
```



No:

Date:

### PROBLEM 4:

The following code is intended to implement a 1:2 de-MUX. The input is  $x$  and two outputs are  $y$  and  $z$ , and the switch control is  $s$ .

```
wire x, y;
reg z;
always @(x or y or z)
begin
    if (!s) y = x;
    else z = x;
end
```

~~Q20~~

a) Find out all the things wrong in this code.

Ans: The following are the things wrong in this code:

1.  $y$  should be declared as reg because it is an output.

~~2. Since  $y$  and  $z$  are outputs, they should not be in the sensitivity list of the always block.~~

2. Since  $y$  and  $z$  are outputs, they should not be in the sensitivity list of the always block.

3.  $s$  should be there in the sensitivity list of the always block.

No:

Date:


b) Does the code produce any latches? If no, state why. If yes, how many latches can be produced? And by which statement(s)?

Ans: Yes, this code produce 2 latches. One to store the previous value of  $z$ , when  $s=0$  and  $y=x$  is executed. And the other to store the previous value of  $y$ , when  $s=1$  and  $z=x$  is executed.

c) After all the problems you find in (a) are fixed, draw the logic diagram of the synthesized hardware from the corrected code.

~~Qazw~~

solutions

 



No:

Date:

### PROBLEM 5:

Below is a short snippet of verilog code of a digital functional block. Draw the logic circuit diagram that is described by the verilog code.

```
module M(Q, S, A, B, C);
```

```
output Q;
```

```
input S, A, B, C;
```

```
reg Q;
```


```
always @(posedge C)
```

```
Q = (S)? A : B;
```

```
endmodule
```

~~Q = 0;~~

Solution:

 



No:

Date:

## PROBLEM 6:

Solution:

```
module Gray_3bit(C, R, OUT);
```

```
input C, R;
```

```
output [2:0] OUT;
```

```
reg [2:0] OUT;
```

```
parameter [2:0] A = 3'b000,
```

```
B = 3'b001, C = 3'b011, D = 3'b010,
```

```
E = 3'b110, F = 3'b111, G = 3'b101,
```

```
H = 3'b100; 3'b000
```

```
always @(posedge C)
```

```
if (R)
```

```
OUT = 3'b000;
```

```
else
```

```
case(OUT)
```

```
A: OUT = B;
```

```
B: OUT = C;
```

```
C: OUT = D;
```

```
D: OUT = E;
```

```
E: OUT = F;
```

```
F: OUT = G;
```

```
G: OUT = H;
```

```
H: OUT = A;
```

```
default: OUT = A;
```

```
endcase
```

```
endmodule
```

No:

Date:

## PROBLEM 7:

Raza

Solution:

```
module Mux8to1(S, I0, I1, I2, I3, I4, I5, I6, I7, O);  
    input [2:0] S;  
    input [7:0] I0, I1, I2, I3, I4, I5, I6, I7;  
    output [7:0] O;  
    reg [7:0] O;  
  
    always @(*)  
        case(S)  
            3'b000: O = I0;  
            3'b001: O = I1;  
            3'b010: O = I2;  
            3'b011: O = I3;  
            3'b100: O = I4;  
            3'b101: O = I5;  
            3'b110: O = I6;  
            3'b111: O = I7;  
        endcase  
    endmodule
```

No:

Date:

## PROBLEM 8 :

Solution :

*Qaza*

```
module Design(C, R, D0, D1, D2, D3, D4, D5, D6, D7, OUT);  
    input C, R;  
    input [7:0] D0, D1, D2, D3, D4, D5, D6, D7;  
    output [7:0] OUT;
```

```
    wire [3:0] GOUT;
```

```
    C74ay 3bit    gC1(C, R, GOUT);  
    Mux 8to1     m1(GOUT, D0, D1, D2, D3, D4, D5,  
                    D6, D7, OUT);
```

```
endmodule
```