

CSE-308: Digital System Design

Lecture 3

VERILOG

Hardware Description Language

About Verilog

- Along with VHDL, Verilog is among the most widely used HDLs.
- Main differences:
 - VHDL was designed to support system-level design and specification.
 - Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.
- The differences become clear if someone analyzes the language features.

- **VHDL**
 - Provides some high-level constructs not available in Verilog (user defined types, configurations, etc.).
- **Verilog**
 - Provides comprehensive support for low-level digital design
 - Not available in native VHDL
 - Range of type definitions and supporting functions (called packages) needs to be included.

Concept of Verilog "Module"

© CET
I.I.T. KGP

- In Verilog, the basic unit of hardware is called a module.
 - Modules cannot contain definitions of other modules.
 - A module can, however, be instantiated within another module.
 - Allows the creation of a *hierarchy* in a Verilog description.



Basic Syntax of Module Definition


CCET
GP

module module_name (list_of_ports);


input/output declarations //

local net declarations //

Parallel statements //

 

endmodule

 

Example 1 :: simple AND gate


10 CET
T. KGP

```
module simpleand (f, x, y);  
  input x, y;  
  output f;  
  assign f = x & y;  
endmodule
```

Example 2 :: two-level circuit

10 CET
T. KGP

```
module two_level (a, b, c, d, f);  
  input a, b, c, d;  
  output f;  
  wire t1, t2;  
  assign t1 = a & b;  
  assign t2 = ~(c | d);  
  assign f = t1 ^ t2;  
endmodule
```

 

Example 3 :: a hierarchical design

```
module add3 (s, cy3, cy_in, x, y);  
    input [2:0] x, y; //  
    input cy_in; //  
    output [2:0] s; //  
    output cy3; //  
    wire [1:0] cy_out; //  
    add B0 (cy_out[0], s[0], x[0], y[0], cy_in);  
    add B1 (cy_out[1], s[1], x[1], y[1], cy_out[0]);  
    add B2 (cy3, s[2], x[2], y[2], cy_out[1]);  
endmodule
```

Specifying Connectivity

© CET
I.I.T. KGP

- There are two alternate ways of specifying connectivity:

- Positional association

- The connections are listed in the same order

add A1 (c_out, sum, a, b, c_in);

- Explicit association

- May be listed in any order

add A1 (.in1(a), .in2(b), .cin(c_in),
.sum(sum), .cout(c_out));

Variable Data Types

© CET
I.I.T. KGP



- A variable belongs to one of two data types:
 - Net
 - Must be continuously driven
 - Used to model connections between continuous assignments & instantiations
 - Register
 - Retains the last value assigned to it
 - Often used to represent storage elements

~~D net f~~



Net data type

- Different 'net' types supported for synthesis:
 - wire, wor, wand, tri, supply0, supply1
- 'wire' and 'tri' are equivalent; when there are multiple drivers driving them, the outputs of the drivers are shorted together.
- 'wor' / 'wand' inserts an OR / AND gate at the connection.
- 'supply0' / 'supply1' model power supply connections.


wire $f1, f2$;

  

wand $f1$;

  


```
module using_wire (A, B, C, D, f);  
  input  A, B, C, D;  
  output f;  
  wire  f;          // net f declared as 'wire'  
  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```

 

```
module using_wired_and (A, B, C, D, f);  
  input  A, B, C, D;  
  output f;  
  wand f;           // net f declared as 'wand'  
  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```


 
```
module using_supply_wire (A, B, C, f);  
  input  A, B, C;  
  output f; → wire t1, t2;  
  supply0 gnd;  
  supply1 vdd;  
  nand G1 (t1, vdd, A, B);  
  xor G2 (t2, C, gnd);  
  and G3 (f, t1, t2);  
endmodule
```



Register data type

- Different 'register' types supported for synthesis:

- reg, integer

- The 'reg' declaration explicitly specifies the size.

- reg x, y; // single-bit register variables

- reg [15:0] bus; // 16-bit bus, bus[15] MSB

- For 'integer', it takes the default size, usually 32-bits.

- Synthesizer tries to determine the size.

Other differences:

- In arithmetic expressions,
 - An 'integer' is treated as a 2's complement signed integer.
 - A 'reg' is treated as an unsigned quantity.
- General rule of thumb
 - 'reg' used to model actual hardware registers such as counters, accumulator, etc.
 - 'integer' used for situations like loop counting.

module simple_counter (clk, rst, count);

input clk, rst;

output count;

reg [31:0] count;

always @(posedge clk)

begin

if (rst)


count = 32'b0;

else

count = count + 1;

end

endmodule

 

$$\begin{array}{r} 01111111 \\ + 1 \\ \hline 10000000 \end{array}$$

- When 'integer' is used, the synthesis system often carries out a data flow analysis of the model to determine its actual size.

- Example:

wire [1:10] A, B;

integer C;

[C = A + B;

$$\begin{array}{r} A \Rightarrow 10 \\ B \Rightarrow 10 \\ \hline 10+1 \end{array}$$

→ The size of C can be determined to be equal to 11 (10 bits plus a carry).

Specifying Constant Values

© CET
I.I.T. KGP

- A value may be specified in either the 'sized' or the 'un-sized' form.

– Syntax for 'sized' form:

<size>'<base><number>

32'b0

- Examples:

8'b01110011 // 8-bit binary number

12'hA2D // 1010 0010 1101 in binary

12'hCx5 // 1100 xxxx 0101 in binary

25 // signed number, 32 bits

1'b0 // logic 0

1'b1 // logic 1